

AMERICAN INTERNATIONAL UNIVERSITY BANGLADESH



Assignment Cover Sheet

Students must complete all details except the faculty use part.

Please submit all assignments to your subject lecturers or the office of the concerned lecturer.

Assignment Title: Study of Zener Diode
 Assignment Number: 04 Due Date: _____ Semester: Fall 22-23
 Subject Code: _____ Subject Name: ED Lab Section: C
 Course Instructor: Dr. MD. Shiduyaman Degree Program: EEE

Declaration and Statement of Authorship:

- I/we hold a copy of this assignment, which can be produced if the original is lost/ damaged.
- This assignment is my/our original work and no part of it has been copied from any other student's work or from any other source except where due acknowledgement is made.
- No part of this assignment has been written for me/us by any other person except where such collaboration has been authorized by the lecturer/teacher concerned and is clearly acknowledged in the assignment.
- I/we have not previously submitted or currently submitting this work for any other course/unit.
- This work may be reproduced, communicated, compared and archived for the purpose of detecting plagiarism.
- I/we give permission for a copy of my/our marked work to be retained by the School for review and comparison, including review by external examiners.

I/we understand that

- Plagiarism is the presentation of the work, idea or creation of another person as though it is your own. It is a form of cheating and is a very serious academic offence that may lead to expulsion from the University. Plagiarized material can be drawn from, and presented in, written, graphic and visual form, including electronic data, and oral presentations. Plagiarism occurs when the origin of the material used is not appropriately cited.
- Enabling plagiarism is the act of assisting or allowing another person to plagiarize or to copy your work.

Group Name (if applicable): C7

No.	Student Name	Student Number	Student Signature	Date
1	<u>Ante Das (C)</u>	<u>20-44112-2</u>	<u>Ante</u>	
2	<u>Sorjarn Hossain Satat</u>	<u>20-4365-2</u>	<u>Satit</u>	
3	<u>Tunayed Alam Albee</u>	<u>20-44034</u>	<u>Alba</u>	
4	<u>Md. Imtiaz Hossain (C)</u>	<u>19-41203-2</u>	<u>Imtiaz</u>	
5	<u>Shaiat Ali</u>	<u>17-338292</u>	<u>Shait</u>	
6				

For faculty use only:

Total Marks: _____ Marks Obtained: _____

Faculty comments _____

8

Title: Study of Zener Diode

Abstract: A Zener Diode is a diode that allows current to flow in forward direction in the same way that an ideal diode does, but also allows it to flow in the reverse direction when a voltage exceeds a certain value known as the breakdown voltage Zener knee voltage Zener voltage avalanche point or peak inverse voltage.

Introduction: The main object is to study the voltage-current characteristics of Zener diode and observe the voltage regulation characteristics of a Zener Diode.

Theory and Methodology: The fundamental purpose of a Zener diode is to maintain a particular voltage across its terminals within specified limitations of time or load variation. It is typically used to provide a steady reference voltage for power supply and other device.

A Zener diode is similar to a regular diode with the difference that it is put in the circuit in reverse biased and functions in reverse breakdown. The operation range of a Zener is illustrated by this typical characteristics curve. It is worth noting that its forward properties are identical to those of standard diode.

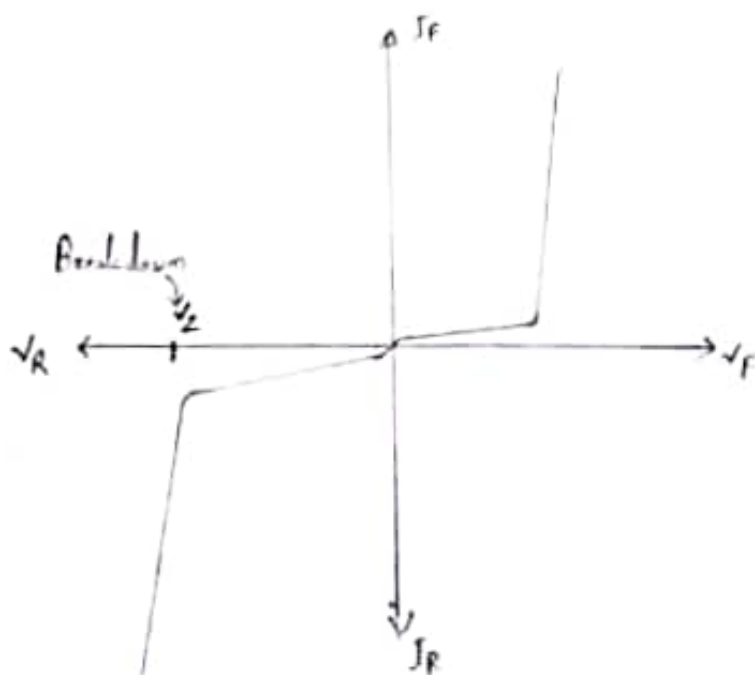


Figure: The normal operating for a Zener diode is shaded.

The breakdown properties of the Zener diode are determined by the doping procedure. Zener with a

voltage less than 5V operate in the Zener break-down range. Those intended to function at more than 5V are generally in the avalanche breakdown range. Zener with voltage breakdowns ranging from 1.5V to 200V are available.

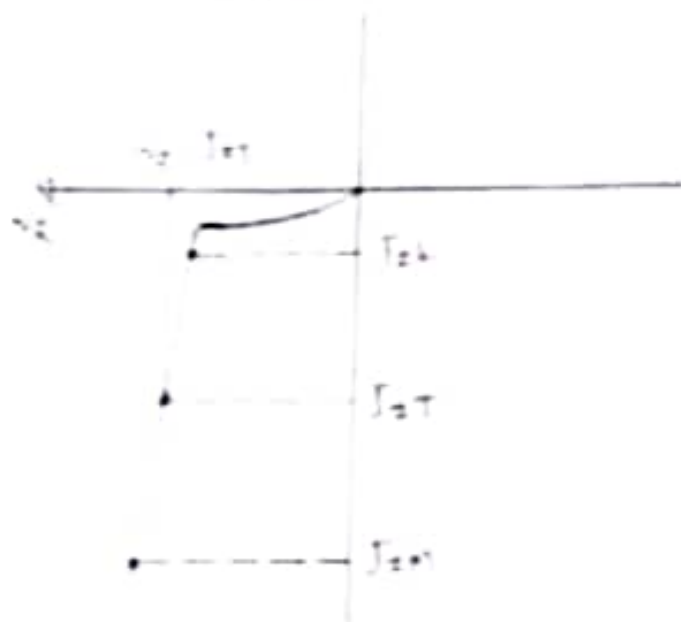


Figure: This curve illustrates the minimum and maximum ranges of current operation that the Zener can effectively maintain its voltage.

A voltage regulator is intended to maintain the output voltage of a circuit constant at a circuit irrespective of the input voltage and the load current.

The simplest version of such a voltage regulation circuit depicted in figure in the circuit Diagram section is a Zener diode linked in parallel to the load. When the voltage across the load attempts to climb the Zener diode draws more current. This increase in current through the resistor produces a rise in the voltage dropped across the resistor, causing the voltage across the load to stay constant. Similarly if the voltage across the load attempts to decline the Zener diode draws less current. Both current through the resistor and the voltage across the resistor decrease. The voltage across the load stays unchanged.

Apparatus:

- 1) Zener Diode
- 2) Trainer Board
- 3) Resistors (100Ω , 220Ω , 470Ω)
- 4) Oscilloscope
- 5) Multimeter
- 6) chond
- 7) POT $100k\Omega$
- 8) DC power supply.

Circuit diagram:

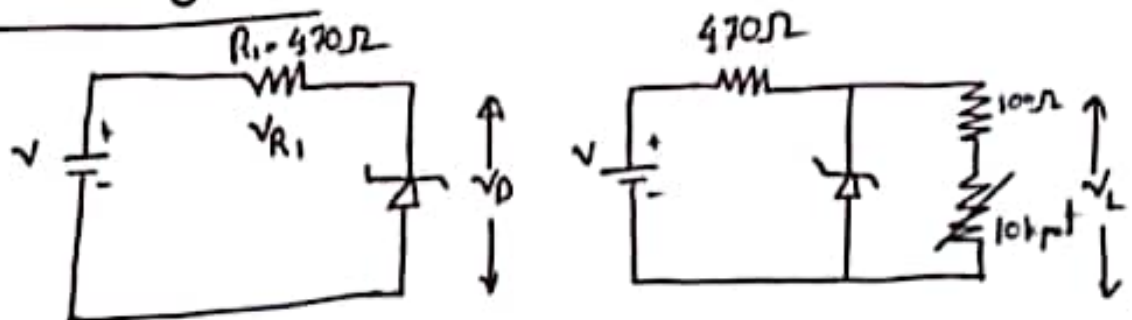


Figure: Zener circuit

Experimental Procedure:

1. All the circuit were connected as shown in the diagram
2. By varying the supply voltage necessary data was taken to complete table 1.
3. The POT was kept at maximum resistance position and the circuit was powered up
4. The POT resistance was gradually decreased and then table 2 was complete
5. The pot was kept at lowest resistance position when varying the supply voltage and reading for table number 3 was taken.

V	V_{R_1}	V_Z	$I = (V_{R_1}/R_1)$
3.5	0	5.61	0
4.5	0	5.53	0
5.5	0.01	5.55	0.00002
6.5	0.93	5.62	0.0041
7.5	1.95	5.63	0.0062
8.5	2.91	5.64	0.0071
9.5	3.94	5.65	0.0104
10.5	4.9	5.65	0.0121
11.5	5.7	5.66	0.0136
12.5	6.70	5.67	0.0142
13.5	7.83	5.68	0.0169

Table: Data for $V-I$ characteristics.

V_R (mV)	100	300	500	700
V_L	5.65	5.64	5.64	5.65
$I_L = (V_L/R_L)$	1.522	1.934	1.986	2.125

Table: Data for regulation due to load voltage

V	16	12	9	6
V_R	.10	.10	.10	.10
V_L	5.69	5.66	5.64	5.59

Table: Data for regulation due to supply voltage regulation.

Simulation & Measurement:

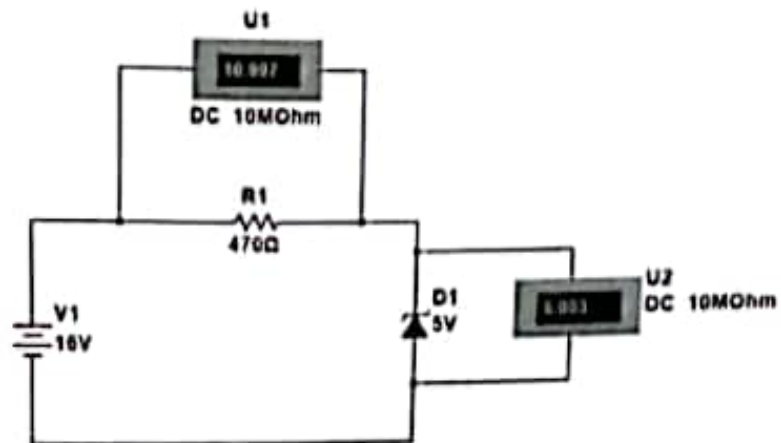


Figure 1

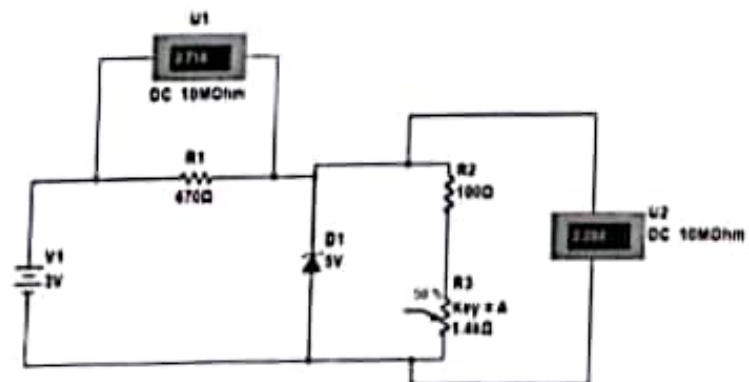


Figure 2

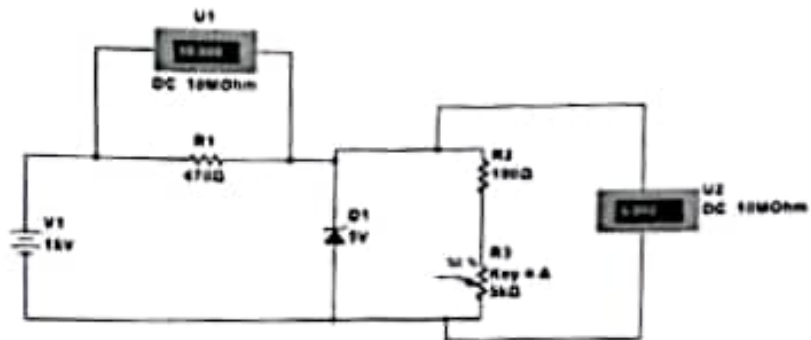


Figure 3

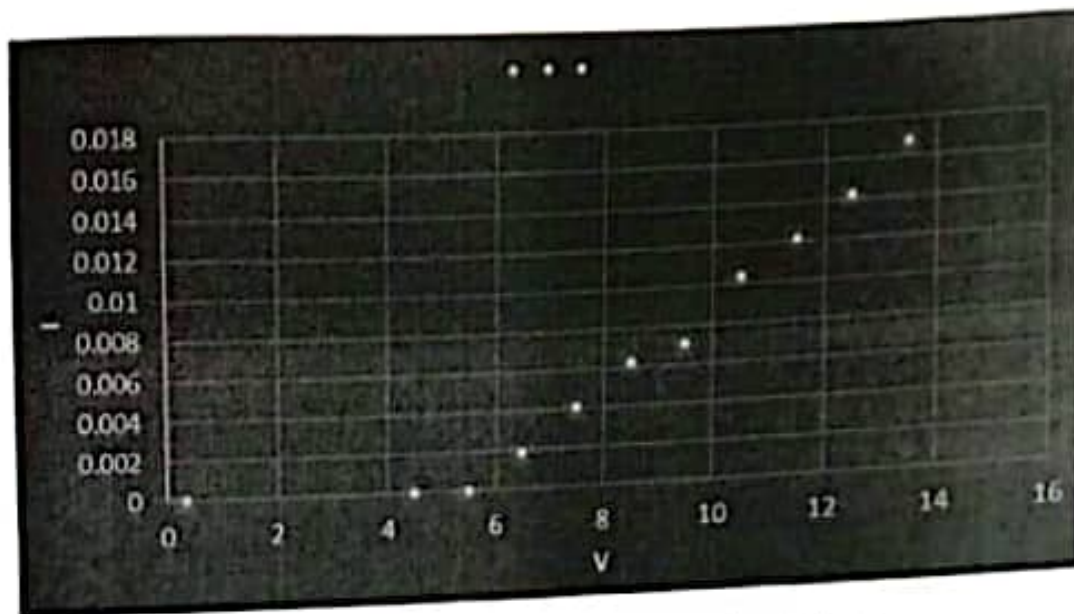


Figure: Data for Regulation due to load variation.


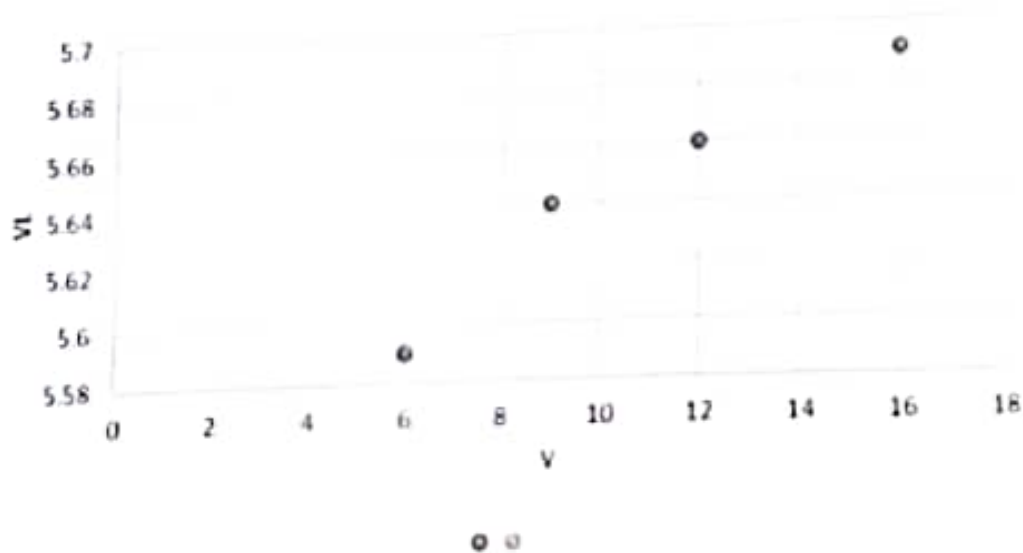
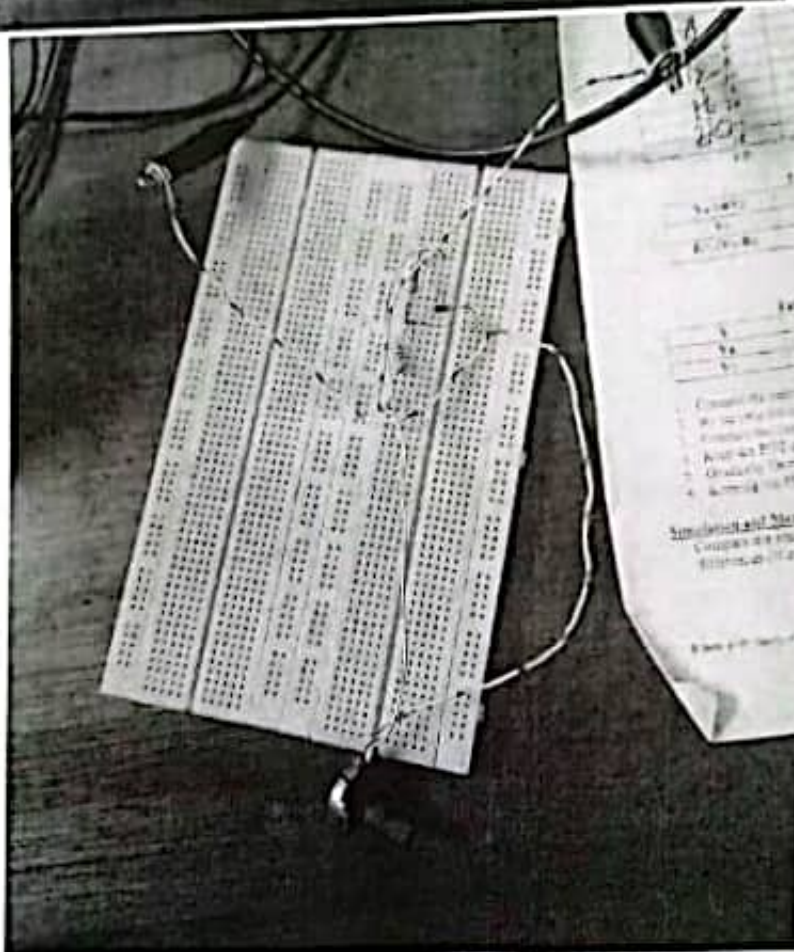


Figure: Data for regulation due to supply voltage variation.

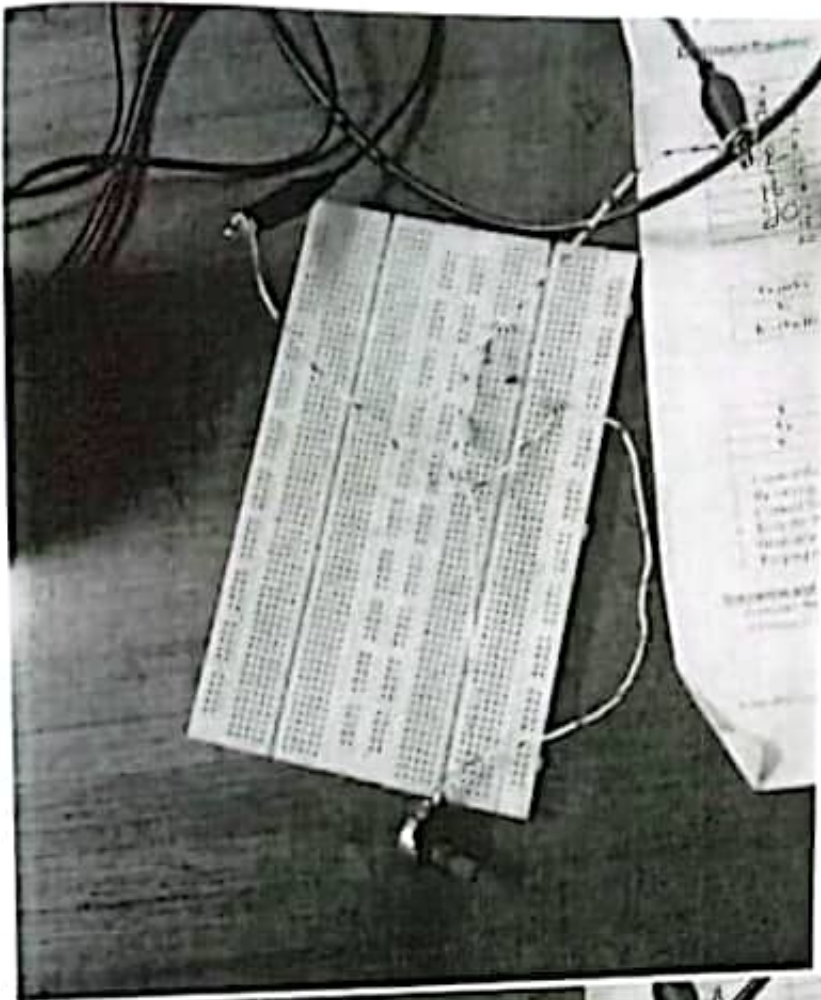

Discussion and Conclusion: Interpret the data findings and determine the extent to which the experiment was successful in complying with the goal that was initially set.

Discuss any mistake that might have been made while conducting the investigation and describe ways the study could have been improved.

References:

1. Adel S. Sedra, Kenneth C. Smith, "Microelectronic Circuit", Saunders College Publishing, 3rd ed., ISBN: 0-03-051648-X, 1991
2. David J. Comer, Donald T. Comer, Fundamentals of Electronic Circuit Design John Wiley and Sons Canada, Ltd; ISBN: 0471410160, 2002
3. American International University - Bangladesh (AIUB) Electronic LAB Manual.