

**AMERICAN INTERNATIONAL UNIVERSITY BANGLADESH**  
**Faculty of Engineering**  
**Laboratory Report Cover Sheet**



*Students must complete all details except the faculty use part.*

Please submit all reports to your subject supervisor or the office of the concerned faculty.

Laboratory Title: Bipolar Junction Transistor (BJT) study of single stage Transistor common emitter  
 Experiment Number: 07 Due Date: 22/11/22 Semester: Fall 2022-23  
 Subject Code: EEE Subject Name: Electronic Device Lab Section: C  
 Course Instructor: Dr. Md. Muhammad Shihjuman Degree Program: BSc. EEE  
BSc. CSE

**Declaration and Statement of Authorship:**

- I/we hold a copy of this report, which can be produced if the original is lost/ damaged.
- This report is my/our original work and no part of it has been copied from any other student's work or from any other source except where due acknowledgement is made.
- No part of this report has been written for me/us by any other person except where such collaboration has been authorized by the lecturer/teacher concerned and is clearly acknowledged in the report.
- I/we have not previously submitted or currently submitting this work for any other course/unit.
- This work may be reproduced, communicated, compared and archived for the purpose of detecting plagiarism.
- I/we give permission for a copy of my/our marked work to be retained by the School for review and comparison, including review by external examiners.

**I/we understand that**

- Plagiarism is the presentation of the work, idea or creation of another person as though it is your own. It is a form of cheating and is a very serious academic offence that may lead to expulsion from the University. Plagiarized material can be drawn from, and presented in, written, graphic and visual form, including electronic data, and oral presentations. Plagiarism occurs when the origin of the material used is not appropriately cited.
- Enabling plagiarism is the act of assisting or allowing another person to plagiarize or to copy your work

Group Number (if applicable): 07 ☐ Individual Submission ☒ Group Submission

No.	Student Name	Student Number	Student Signature	Date
Submitted by:				
1	<u>Md Imtiaz Hossain</u> (C)	<u>19-41203-2</u>	<u>[Signature]</u>	
Group Members:				
2	<u>Arta Das</u> (C)	<u>20-44112-2</u>	<u>[Signature]</u>	
3	<u>Ali Shuaib</u>	<u>17-35829-1</u>	<u>[Signature]</u>	
4	<u>Sajjam Hossain Safat</u>	<u>20-43653-2</u>	<u>[Signature]</u>	
5	<u>Tunayed Alam Albee</u>	<u>20-44031-2</u>	<u>[Signature]</u>	

For faculty use only:

Total Marks: \_\_\_\_\_ Marks Obtained: \_\_\_\_\_

Faculty comments \_\_\_\_\_



Title: Bipolar Junction Transistor (BJT): Study of single stage transistor Amplifier.

Introduction: The aim of the ac analysis is to determine the voltage amplification ( $A_v$ ), current amplification ( $A_i$ ), input impedance ( $Z_i$ ), output impedance ( $Z_o$ ), and the phase relation between the input voltage ( $V_i$ ) and the output voltage ( $V_o$ ). After performing the dc analysis, we will now calculate the small signal parameters depending on the model being used, draw the small signal equivalent circuit and then perform the ac analysis.

The main objectives of this experiment are to -

1. Trace the circuit diagram of a single stage transistor Amplifier;
2. Measure Beta ( $\beta$ ) of the transistor with multimeter.

3. Measure the Q-point.
4. Measure the maximum signal that can be amplified with the amplifier without any distortion.
5. Measure the maximum voltage gain of the amplifier at 1 KHz.
6. Measure the voltage gain of the amplifier at different values of load resistance.

Theoretical Background: The analysis is done assuming that the signal frequency is sufficiently high. Subsequently it can be assumed that all the coupling capacitors (CE) act as perfect short circuit. Such a frequency is said to be in the mid band of the amplifier.

The hybrid- $\pi$  model and T-model can be valid only for small signals. The general forms of these models are shown in the following figures 1 and 2.



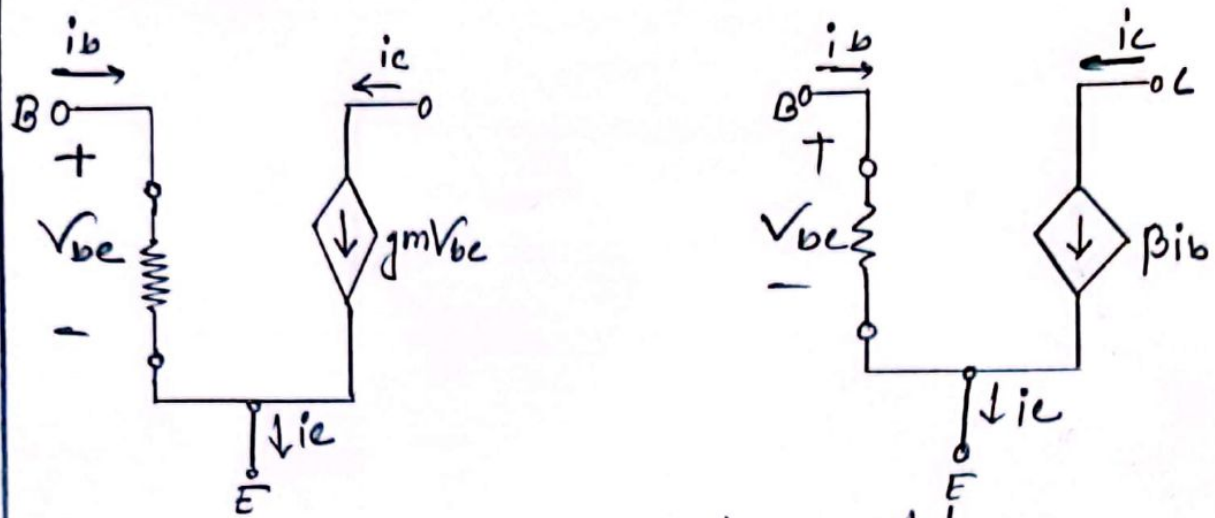


Fig: 1 The Hybrid  $\pi$ -model

Where, Transconductance

$$g_m = \frac{I_c}{V_T} \text{ and } V_T = \frac{KT}{q}$$

Common emitter input resistance

$$r_{\pi} = \frac{\beta}{g_m}$$

Common base input resistance.

$$r_e = \frac{\alpha}{g_m}$$

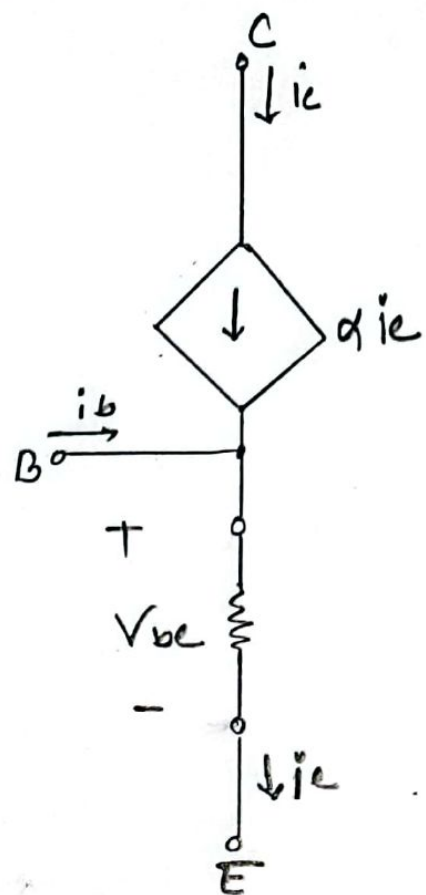
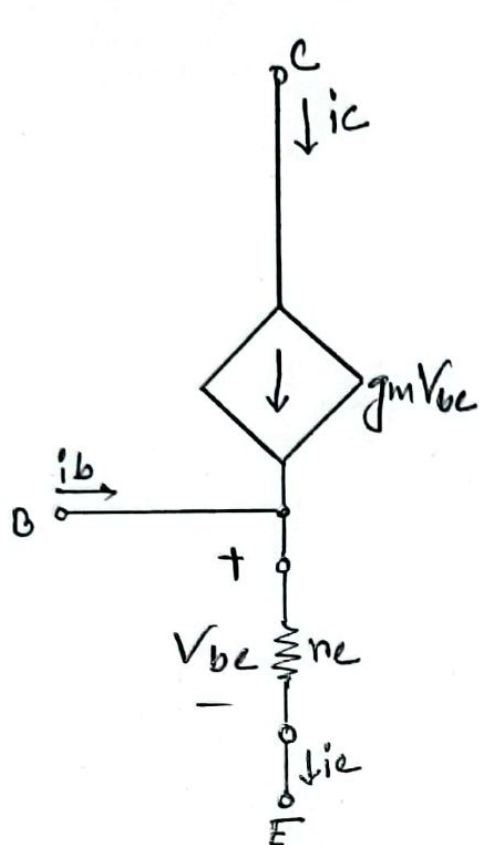


Fig:2 The T-model

Since in this experiment we will mainly concentrate on single stage amplifiers where most widely used single transistor amplifiers in common emitter configuration is shown in the figure below.

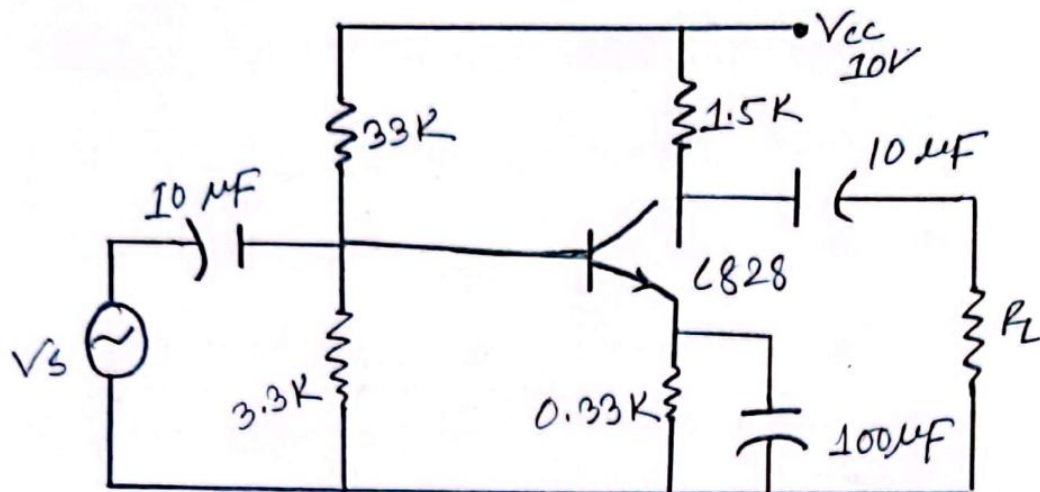


Fig: 3 Single Stage CE Amplifier.

### Apparatus:

No	Apparatus	Quantity
1.	Transistor (C828)	1
2.	33K, 10K, 4.7K, 1K, 3.3K, 1.5K, 330Ω	1 for each Resistor
3.	Project Board	1
4.	Cathode Ray Oscilloscope (CRO)	1
5.	Multimeter	1
6.	Signal Generator	1
7.	100 μF capacitor	1
8.	Probes	2
9.	Power supply cable	2



Precaution: Transistors are sensitive to be damaged by electrical overloads, heat, humidity and radiation. Damage of this nature often occurs by applying the incorrect polarity voltage to the collector circuit or excessive voltage to the input circuit. One of the most frequent causes of damage to a transistor is the electrostatic discharge from the human body when the device is handled.

### Experimental Procedure:

1. Measure  $\beta$  of the transistor with multimeter.
2. Calculate DC operating point of the transistor circuit.
3. Implement the circuit as shown in the figure.
4. Measure the operating point with the help of table: 1 and compare with your calculate value.

5. Feed an ac signal of 1 KHz at the input and observe the input and output on the CRO.
6. Increase the input signal till the output wave shape starts getting distorted.  
Measure this input signal. This is the maximum input signal that the amplifier can amplify without any distortion.
7. Now feed an ac signal that is less than the maximum signal handling capacity of the amplifier. Fix the input signal frequency at 1 KHz, Draw the input and output voltage wave shape and calculate gain.
8. Connect different load resistors and find the voltage gain of the amplifier for each.

Observations:

1. Q-point of the amplifier:

$V_{CC}$	$V_C$	$V_{CC} - V_C$	$I_C = (V_{CC} - V_C) / R_C$	$V_{CC}$
10V	8.69V	1.29V	4.93 mA	8.40V



2. Maximum signal that can be handled by the amplifier without introducing distortion = 50 V and Operating frequency = 50 KHz.

3. Voltage Gain of the Amplifier:

Load resistor	Input Voltage	Output voltage	Gain
1K	410 mV	3V	1.31 ✓
4.7 K	410 mV	4.26 V	10.39 ✓
10 K	410 mV	4.88 V	11.91 ✓
100 K	410 mV	4.78 V	11.65 ✓

Calculation:

$$I_C = (V_{CC} - V_C) / R_C$$

$$= 8.607$$

$$\text{Gain} = \frac{\text{Output}}{\text{Input}}$$

## Simulation and Measurement:

Table 1:

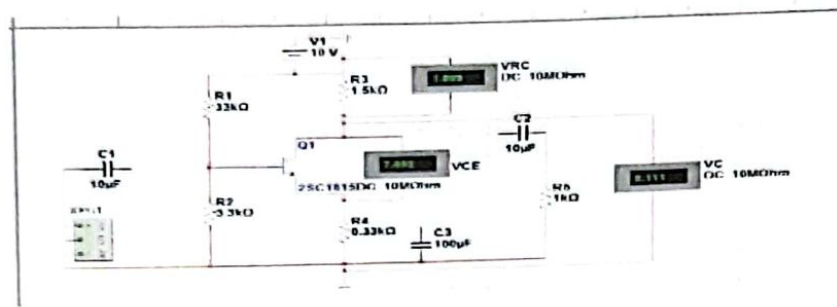


Fig: 4

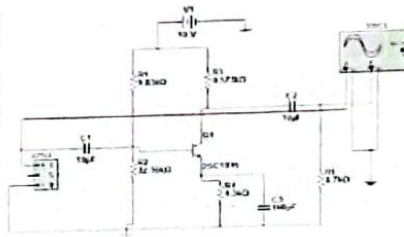
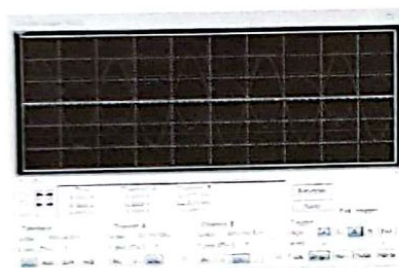


Fig: 5

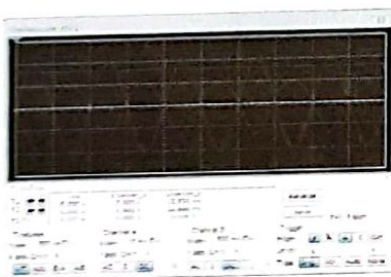


Fig: 6

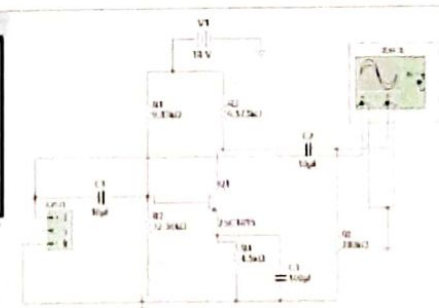


Fig: 7



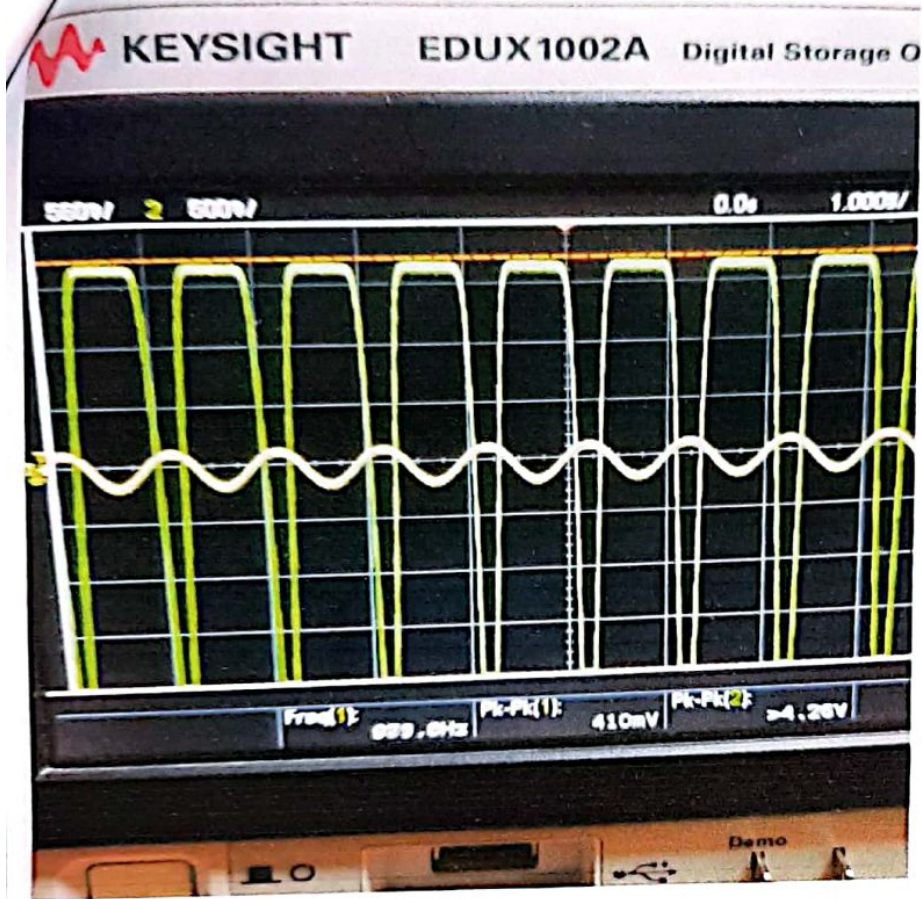


Fig: single stage CE Amplifier wave

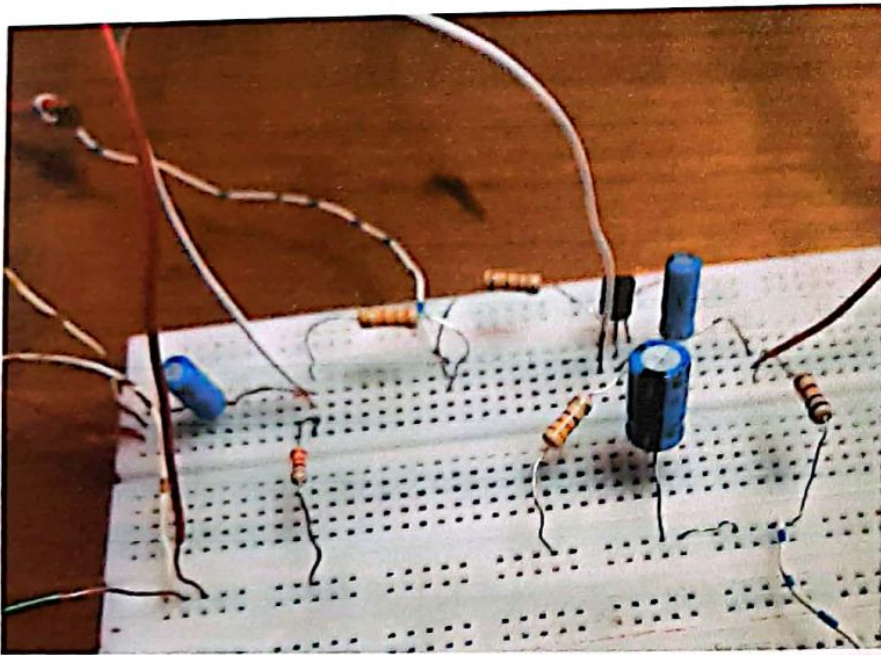


Fig: single stage CE Amplifier

### Discussion:

1. The dc power source needs to be switched off while changing the transistors.
2. The trainer board needs to be checked if working properly.
3. The circuit was connected properly and was also checked before taking the readings.

### References:

1. American International University-Bangladesh (AIUB) Electronic Devices Lab manual.
2. A.S. Sedra, K.C. Smith, "Microelectronic Circuits" Oxford University Press (1998).
3. J. Keown, ORCAD PSpice and circuit Analysis Prentice Hall Press (2001)
4. P. Horowitz, W. Hill, "The Art of Electronics," Cambridge University press (1989).