

AMERICAN INTERNATIONAL UNIVERSITY BANGLADESH  
Faculty of Engineering

Laboratory Report Cover Sheet



Students must complete all details except the faculty use part.

Please submit all reports to your subject supervisor or the office of the concerned faculty.

Laboratory Title: Study of Transistor Characteristics in Common Emitter Amplifier  
Experiment Number: 5 Due Date: \_\_\_\_\_ Semester: Fall 2022-23  
Subject Code: EEE Subject Name: Electronic Device LAB Section: G  
Course Instructor: Dr. Mohammad Shadyjannan Degree Program: BSC. EEE

Declaration and Statement of Authorship:

- I/we hold a copy of this report, which can be produced if the original is lost/ damaged.
- This report is my/our original work and no part of it has been copied from any other student's work or from any other source except where due acknowledgement is made.
- No part of this report has been written for me/us by any other person except where such collaboration has been authorized by the lecturer/teacher concerned and is clearly acknowledged in the report.
- I/we have not previously submitted or currently submitting this work for any other course/unit.
- This work may be reproduced, communicated, compared and archived for the purpose of detecting plagiarism.
- I/we give permission for a copy of my/our marked work to be retained by the School for review and comparison, including review by external examiners.

I/we understand that

- Plagiarism is the presentation of the work, idea or creation of another person as though it is your own. It is a form of cheating and is a very serious academic offence that may lead to expulsion from the University. Plagiarized material can be drawn from, and presented in, written, graphic and visual form, including electronic data, and oral presentations. Plagiarism occurs when the origin of the material used is not appropriately cited.
- Enabling plagiarism is the act of assisting or allowing another person to plagiarize or to copy your work

Group Number (if applicable): (7) ☐ Individual Submission ☒ Group Submission

No.	Student Name	Student Number	Student Signature	Date
Submitted by:				
1	<u>Md Intiq Hossain (C)</u>	<u>19-41203-2</u>		
Group Members:				
2	<u>Antu Das</u>	<u>20-44112-2</u>		
3	<u>Jumayed Alam Akter</u>	<u>20-44031-2</u>		
4	<u>Gujjam Hossain Sifat</u>	<u>20-43653-2</u>		
5	<u>Shajaz Ali</u>	<u>17-33829-1</u>		

For faculty use only:

Total Marks: \_\_\_\_\_ Marks Obtained: \_\_\_\_\_

Faculty comments \_\_\_\_\_

## Title: Study of Transistor Characteristics in Common Emitter Amplifiers.

### Introduction:

A BJT is a three terminal semiconductor device. It is widely used in discrete circuit as well as in integrated circuits. The main applications of BJTs are analog circuit. For example, BJTs are used for amplifiers in particular for high speed amplifiers.

The main objectives of this experiment are to -

1. become familiar with bipolar junction transistor (BJTs).
2. Study the biasing of a common Emitter (CE) Amplifier, and
3. Obtain the input and output characteristics of a common-emitter based BJT circuit.

## Theory and Methodology:

Device structure of bipolar junction transistor  
Each BJT consists of two anti serial connected diodes. The BJT can be either implemented as an npn or a pnp transistor. In both cases the center region forms the base (B) of the transistor, while the external regions form the collector (C) and the emitter (E) of the transistor. External wire connection to the P and n regions (transistor terminals) are made through metal (e.g. Aluminum) contacts.

A cross section of the two types of BJTs consisting of an emitter-base junction and a collector-base junction is shown in the figure below. An npn or a pnp transistor are called bipolar because both types of carriers (electrons and holes) contribute to the

overall current. In the case of a field effect transistor, either the electrons or the holes determine the current flow. Therefore a field effect transistor is a unipolar device. The current and voltage amplification of a BJT is controlled by the geometry of the device (for example width of the base region) and the doping concentrations in the individual regions of the device. In order to achieve a high current amplification, the doping concentration in the emitter region is typically higher than that of the base region. The base is a lightly doped very thin region between the emitter and the collector and it controls the flow of charge carriers from the emitter to collector region.




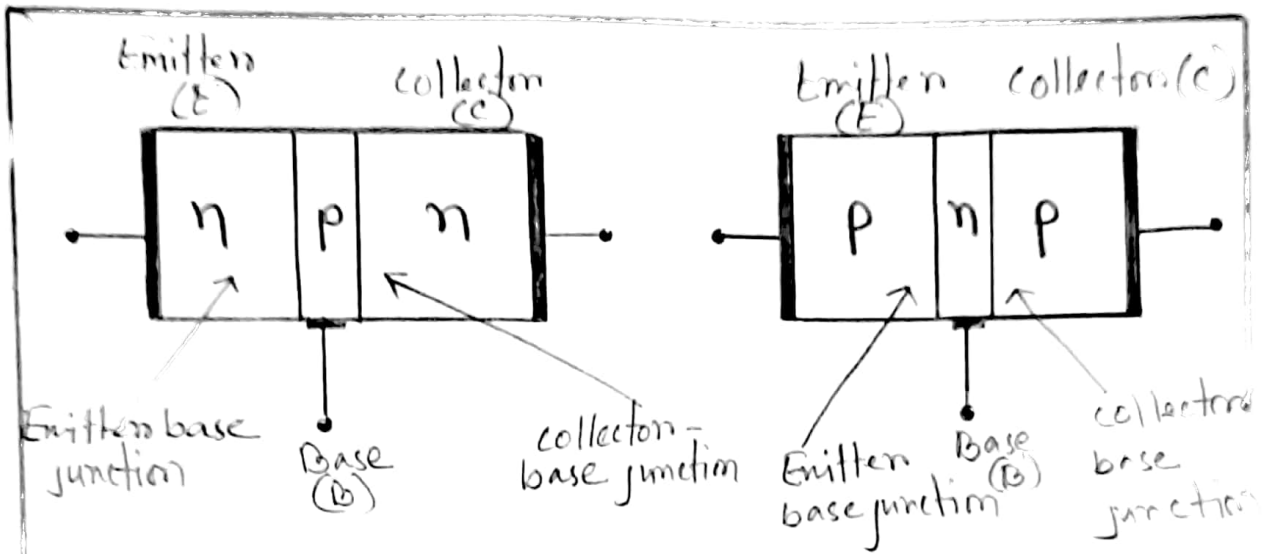



Fig: structure of bipolar transistor.
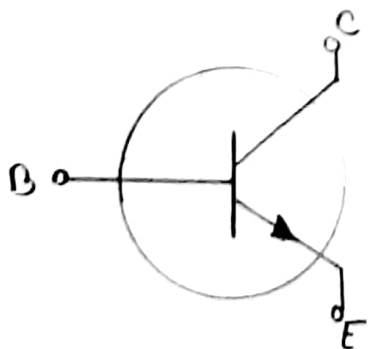
### Circuit Configuration:

The following figures show the symbol for the npn transistor and pnp transistor. The emitter of the BJT is always marked by an arrow which indicates whether the transistor is an npn or a pnp transistor.



npn BJT symbol

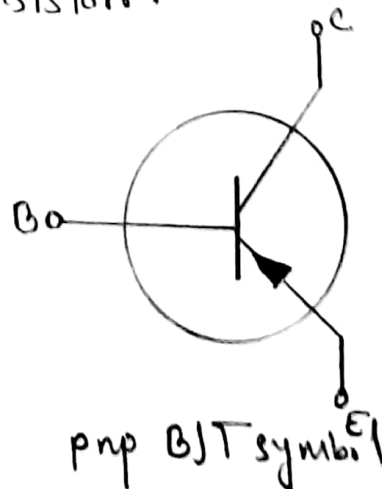

pnp BJT symbol

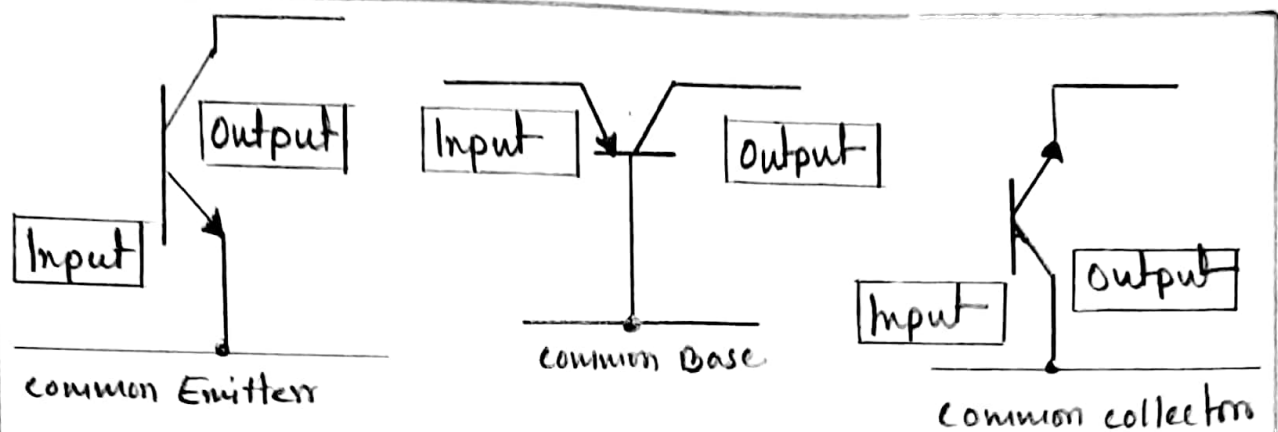


Fig:- Circuit Configuration

There are three basic ways in which a BJT can be configured. In each case, one terminal is common to both the input and output circuit shown in figure above.

1. The common emitter configuration often called an emitter follower, since its output is taken from the emitter resistor. It is useful as an impedance matching device since its input impedance is much higher than its output impedance.
2. The common emitter configuration is used for voltage and current amplification and is the most common configuration for transistors.

amplifiers.

3. The common base configuration is used for high frequency applications because the base separates the input and output minimizing oscillations at high frequency. It has a high voltage gain, relatively low input impedance and high output impedance compared to the common collector.

### Biasing of Bipolar Junction Transistors:

In most of the cases, the BJT is used as an amplifier or switch. In order to perform these functions, the transistor must be correctly biased. Depending on the bias condition (forward or reverse) of each of the BJT junctions, different modes

amplifiers.

3. The common base configuration is used for high frequency applications because the base separates the input and output minimizing oscillations at high frequency. It has a high voltage gain, relatively low input impedance and high output impedance compared to the common collector.

### Biassing of Bipolar Junction Transistors:

In most of the cases, the BJT is used as an amplifier or switch. In order to perform these functions, the transistor must be correctly biased. Depending on the bias condition (forward or reverse) of each of the BJT junctions, different modes



of operation of the BJT are obtained.

There are three modes defined as follows:

1. Active:

Emitter junction is forward biased, collector junction is reverse biased. The BJT operates in the active mode and the BJT can be used as an amplifier.

2. Saturation:

Both the emitter and collector junction are forward biased. If the BJT is used as a switch, the saturation mode corresponds to the on state of the BJT.

3. Cut-off:

Both the emitter and collector junction are reverse biased. If the BJT is used as a switch, the cut-off mode corresponds to the off state of the BJT.

## Apparatus:

1. Trainer board
2. Transistor
3. Resistors (1 K $\Omega$ , 10 K $\Omega$ )
4. DC power supply.
5. Multimeter
6. Power supply cable.

## Precaution:

Transistors are sensitive to be damaged by electrical overloads, heat, humidity, and radiation. Damage of this nature often occurs by applying the incorrect polarity voltage to the collector circuit or excessive voltage to the input circuit. One of the most frequent causes of damage to a transistor is the electrostatic discharge from the human body when the device is handled. The applied voltage, current should not exceed the maximum rating of the given transistor.

### Circuit Diagram:

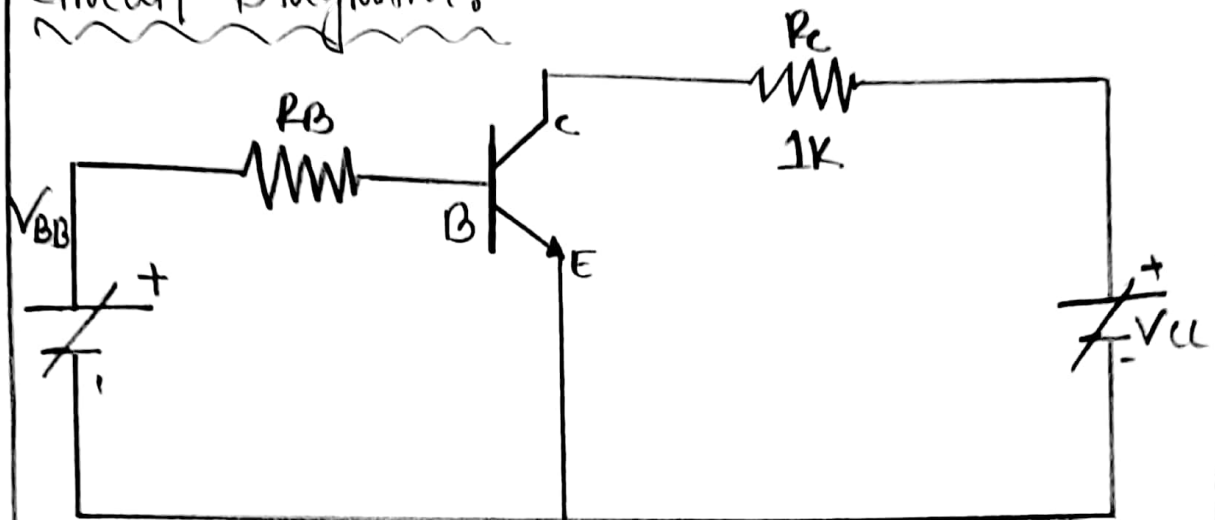


Fig: Transistor Characteristic in CE configuration

### Experimental procedure:

1. The terminals of the transistor were identified
2. The circuit connections were made as shown in the above figure.
3. For input characteristics the voltage  $V_{CE}$  were fixed first and the voltage  $V_{BB}$  were varied and the base current  $I_B$  were calculated.
4. For output characteristics, the input circuit were opened at first (i.e. to make  $I_B = 0$ ). The collector voltage  $V_{CC}$  were varied in

steps of 4V and the collector current  $I_C$  were calculated.

5. Now the input circuit was closed and the base current  $I_B$  was fixed at 50  $\mu A$  by varying  $V_{BB}$ . The voltage  $V_{CC}$  were varied according to the table and  $I_C$  were calculated in each step. The process was repeated for other values of  $I_B$ .

Data Table:

1. Input Characteristics:-

$V_{CC} = 8V$			$V_{CC} = 16V$		
$V_{BB} (V)$	$V_{BE} (V)$	$I_B (A)$	$V_{BB} (V)$	$V_{BE} (V)$	$I_B (mA)$
0	0	0	0	0	0
0.5	0.49	0	0.5	0.49	5
1	0.67	32.3	1	0.67	32.3
1.5	0.68	81.8	1.5	0.76	79.8
2	0.68	131.9	2	0.77	129.9
2.5	0.68	181.9	2.5	0.79	180



$I_B = 0 \mu A$			$I_B = 50 \mu A$			$I_B = 100 \mu A$		
$V_{CC}$	$V_{CE(V)}$	$I_C(mA)$	$V_{CC}$	$V_{CE(V)}$	$I_C(mA)$	$V_{CC}$	$V_{CE(V)}$	$I_C(mA)$
0V	0.49	0	0V	0.01	0.07	0V	0.07	0.017
4V	4.13	0	4V	0.14	3.94	4V	0.11	3.97
8V	8.11	0	8V	0.19	7.96	8V	0.13	8.02
12V	12.09	0	12V	1.82	10.38	12V	0.10	12.08
16V	16.06	0	16V	5.46	10.75	16V	0.19	16.13

### Simulations: (for input characteristics)

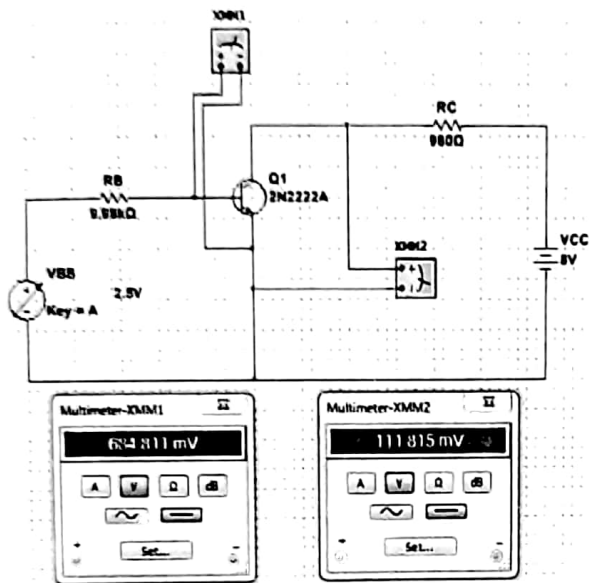


Figure: simulation For 8 volts

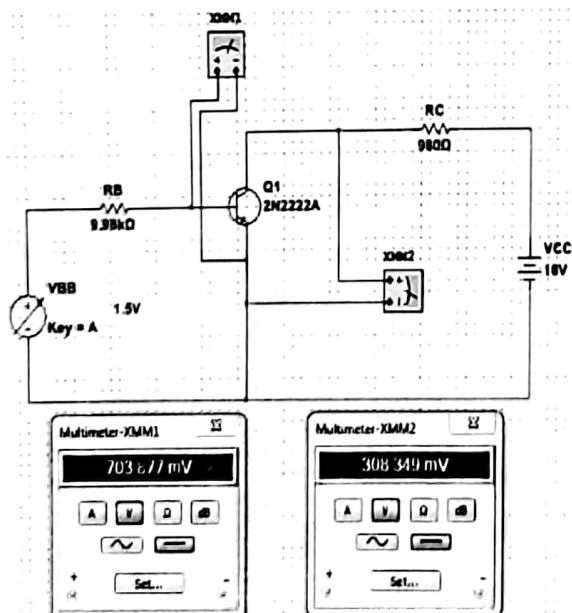


Figure: simulation for 16 volts.

(For output characteristics)

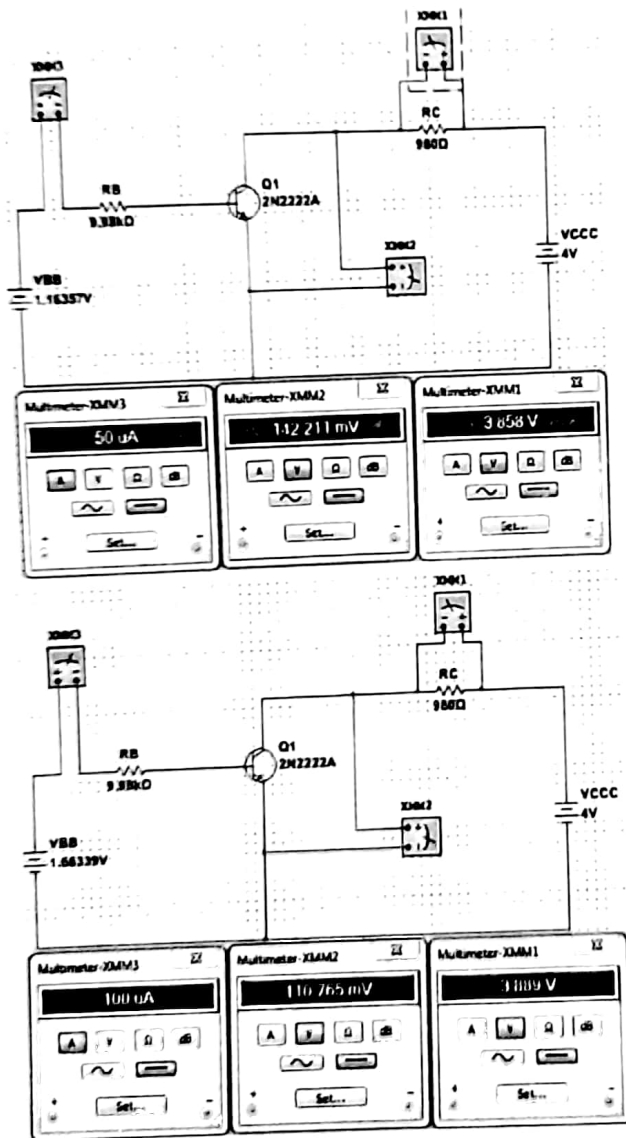


Figure: simulation for 50uA

Figure: simulation For 100uA

### Input characteristics

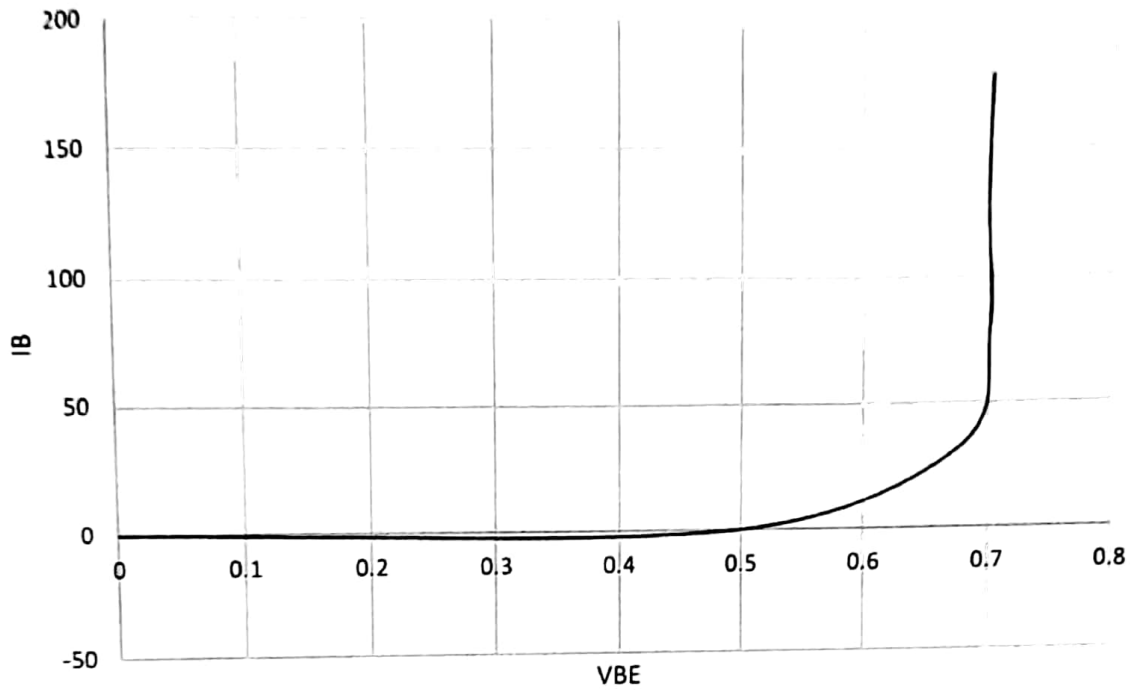


Figure: input characteristics

### Output Characteristics



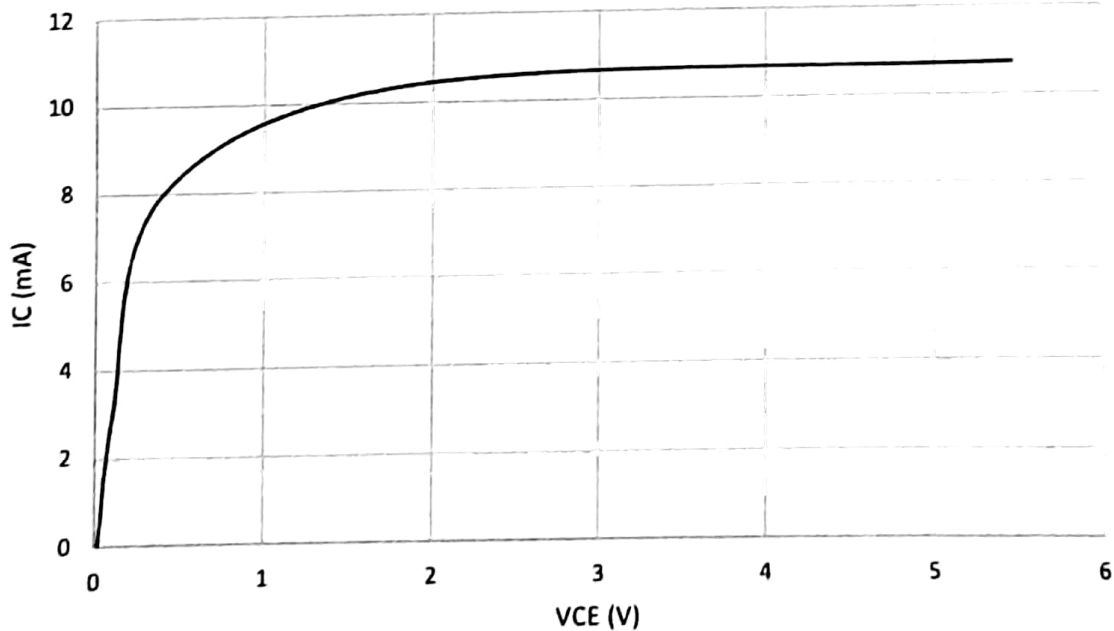


Figure: output characteristics.

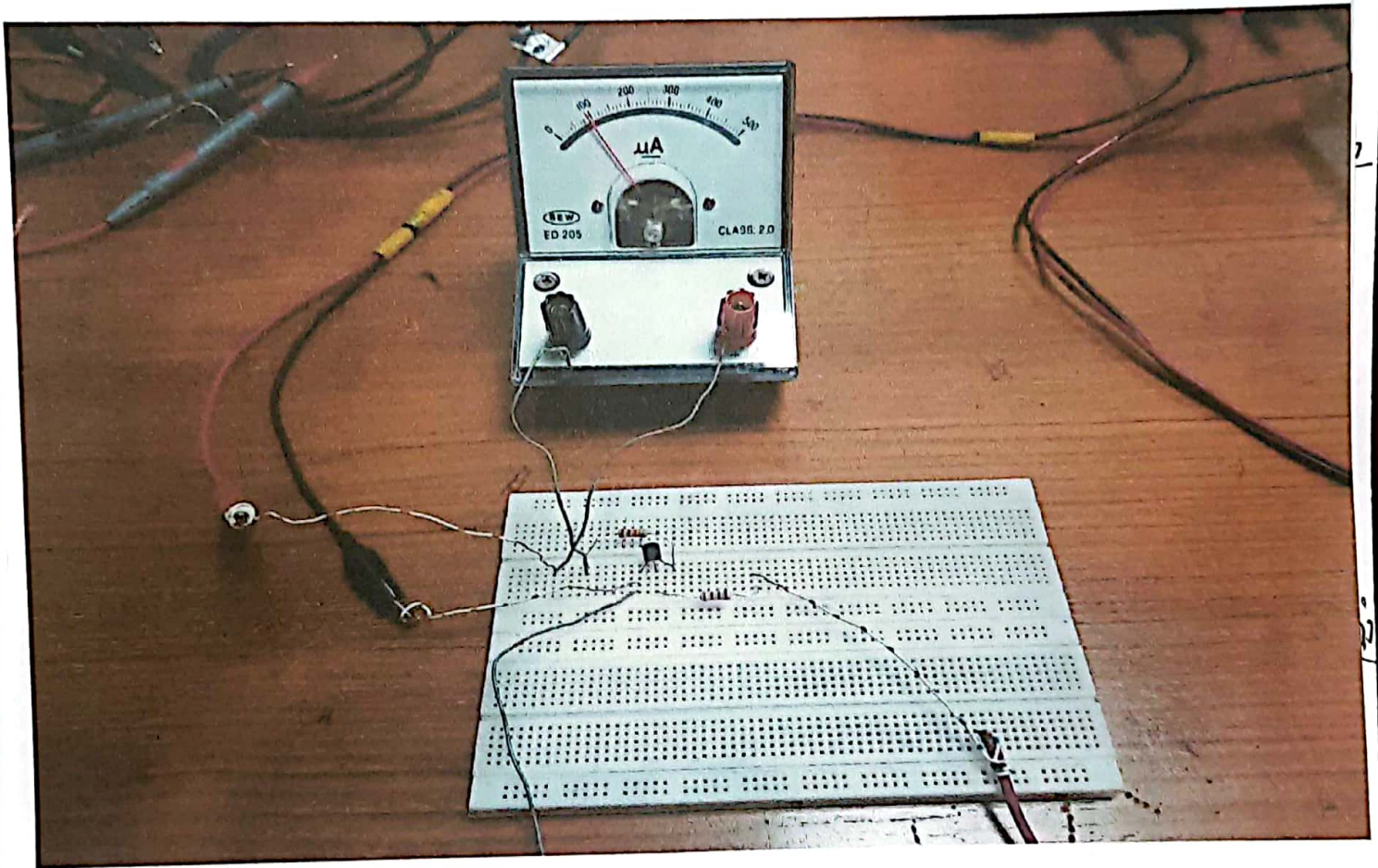

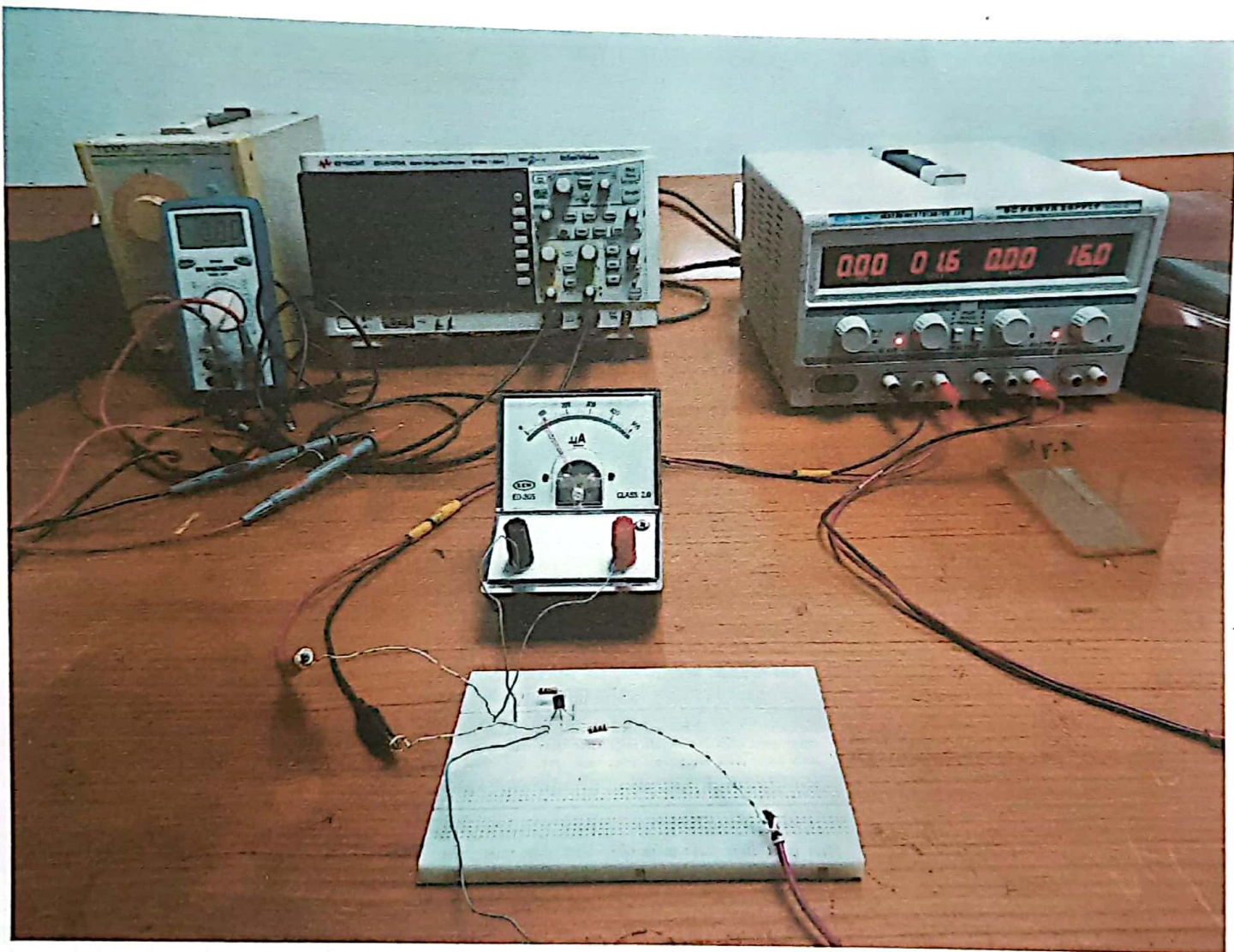





## Discussion and Conclusion:

Interpret the data/findings and determine the extent to the experiment was successful in complying with the goal that was initially set. Discuss any mistake we might have made while conducting the investigation and describe ways study could have been improved.

## Reference(s):

1. Adel S. Sedra Kenneth L. Smith Microelectronic circuit, Saunders college publishing, 3rd ed, ISBN: 0-03-051648-X, 1991.
2. American International University - Bangladesh (AIUB) Electronic Devices Lab Manual.
3. David J. Comer, Donald T. Comer, Fundamentals of Electronic Circuit Design, John Wiley & Sons Canada, Ltd, ISBN: 0471410160, 2002.